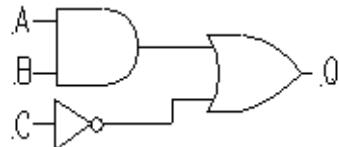



**CS 231: Logic Problems**

- 1) Write an expression for output Q, in terms of the inputs A, B and C:

a)



b)

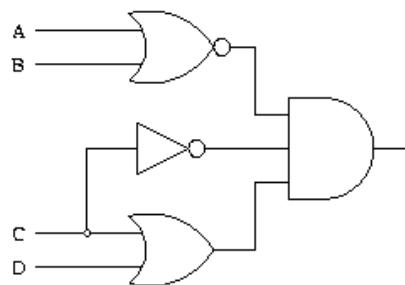

- 2) Draw a Circuit for each expression using AND, OR, and Inverter gates:

a)  $Q = A + B \cdot C$

b)  $Q = AB + \overline{AC}$

c)  $Q = (A+B)(A+C)$

3) For the first expression in Problem 2 :

a. Draw a circuit using only AND and Inverter gates:

b. Write a truth table for the expression, and express Q in Sum of Products and Product of Sums:

4) Simplify the following Expression:  $\overline{AB}(\overline{A} + B)(\overline{B} + B)$


## SOLUTIONS

1) a)  $Q = AB + \overline{C}$


b)  $Q = \overline{(A + B)}(C+D)\overline{C}$

2)


a)

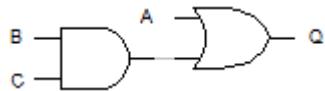

b)

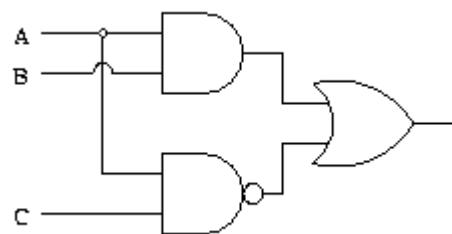


c)

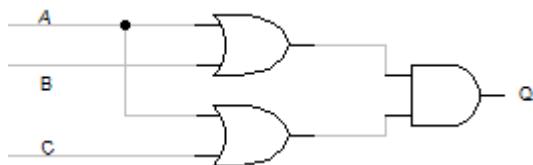

3)

a)

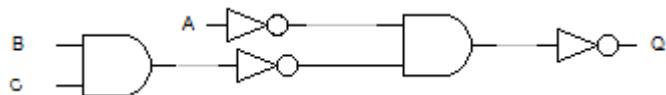

b)

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

SOP (Add minterms):  $Q = \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C + AB\overline{C} + ABC$

POS (Multiply maxterms, minterms of the compliment):  $Q = (A + B + C)(A + B + \overline{C})(A + \overline{B} + C)$

4)  $\overline{AB}(\overline{A} + B)(\overline{B} + B)$

$\overline{AB}(\overline{A} + B)$  Complement Law

$(\overline{A} + \overline{B})(\overline{A} + B)$  DeMorgan's Law

$\overline{A} + \overline{B} B$  Distributive Law

$\overline{A}$  Complement Law